

Class	CS47, Sec 01
Homework	II
Due Date	Apr 25, 2018 11:59 PM PST
Instructions	<ol style="list-style-type: none"> 1. There are 7 questions with total 100 points. 2. Please create electronic document with your answer. 3. There is no need to include the question itself. However, you MUST include question number and sub-part index if any. Example: 5(b) 4. Please create a PDF document <u>hw2.pdf</u> and <u>upload that in Canvas</u> assignment page by the due date. 5. Please re-check you submission for any logistic errors (empty file, corrupted PDF, and many more) and re-submit if needed. Once grading is started, any file with logistics errors will be given 0 point. 6. NO handwritten document is accepted. 7. NO LATE SUBMISSION. 8. Please explain your answer clearly – just writing the final answer in a word or two is not sufficient in most of the cases.

1. Prove the following equation by basic identity rules (mention which rule you have applied; e.g. identity 5).
 - a. $F(a, b, c, d) = (a + b)(a + b + c + d) = a + b$ [10pts.]
 - b. $F(a, b) = ab + a'b' = (a \oplus b)'$ [10pts.]
2. Establish equivalency of Q1 expressions (Q1a & Q1b) by constructing truth table of LHS and RHS. [10 pts.]
3. Write Boolean functions Q1a and Q1b in most compact SOP and POS form. [10pts]
4. Simplify $F(w,x,y,z) = \sum m(0,2,5,7,8,10,13,15)$ using K-map and list all the prime-implicants and essential prime implicants (use compact SOP form). [10pts.]
5. A Boolean function $f(w,x,y,z) = \prod M(1,3,9,11,14) + d(4,5,8,10,12,13)$. List all the prime implicants and essential prime implicants in compact SOP form. [20pts.]
6. Design a rock-paper-scissor digital game. There are four inputs I3, I2, I1, I0 and 3 outputs N, P1, P2. The input pair (I3, I2) encodes selection of player 2 (related to output P2) and input pair (I1, I0) encodes selection of player 1 (related to output P1). The encoding of selection is as following. If any player's setting is '00' output N is 0, P1 is 0 and P2 is 0. For any other setting N is 1, and P1, P2 are 0 or 1 depending on who is winning. If it is a draw, then both P1 and P2 are 1. Show all

the design steps. You should use multi input basic logic gates (e.g. 3-input OR) only (no decoder or multiplexer) **[20pts.]**

Encoding	Selection
00	None
01	Rock
10	Paper
11	Scissor

[Review of rules - paper beats rock, rock beats scissor, scissor beats paper]

7. Design a digital circuit to which value will be input using 5-bit 2's complement form (B4-B0 as input bits). It has following two outputs. **[10pts]**

- DIV3: It will be 1 If input value is completely divisible by 3, 0 otherwise.
- SQR: It will be 1 if absolute of input value is square value, 0 otherwise.